# Tutorial 6. AC and complex valued approach

#### O.M. Kiselev o.kiselev@innopolis.ru

Innopolis university

Impedance Equivalent impedance of serial connected elements Example 1 Impedance of parallel connected elements Example 2 Diagrams and Kirchhoff's laws Summary

・ロト・日本・ヨト・ヨト・日・ つへぐ

### Properties of voltage on elements of circuit



Let us consider serial connection of resistance, capacitor and inductor. In this case for all elements of the circuit the current the same and

 $I=I_0\cos(\omega t).$ 

- The voltage on the resistance:  $V_R = I_0 R \cos(\omega t)$ . The direction coincides to the current.
- ► the voltage on the capacitor:  $V_c = \frac{1}{C} \int_0^t I(t) dt = \frac{I_0}{C} \int_0^t cos(\omega t) dt = \frac{I_0}{C\omega} \sin(\omega t) = R_C I_0 \cos(\omega t \frac{\pi}{2});$
- ► the voltage on the inductor  $V_L = L \frac{dI}{dt} = L I_0 \frac{d}{dt} (\cos(\omega t)) = -L\omega I_0 \sin(\omega t) = R_L I_0 \cos(\omega t + \frac{\pi}{2})$ .

### Vector representation of voltage



The sum of the voltage is equal to external voltage:

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{V},$$

$$an(\phi) = rac{\omega L - rac{1}{\omega C}}{R}.$$

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q @

Here  $\phi$  is the shift between the current and voltage. External voltage:

$$U = U_0 \cos(\omega t + \phi),$$

The triangle:

$$(I_0R)^2 + I_0^2(\omega L - \frac{1}{C\omega})^2 = U_0^2.$$

Then

$$I_0 = \frac{U_0}{\sqrt{R^2 + (\omega L - \frac{1}{C\omega})^2}}.$$

### Complex numbers



Absolute value

$$|z|^2 = x^2 + y^2$$
,  $|z|^2 = z\overline{z} = (x + jy)(x - jy) = x^2 + y^2$ .

Argument

$$\operatorname{Arg}(z) = \begin{cases} \operatorname{arctan}\left(\frac{x}{y}\right), & y > 0; \\ \pi + \operatorname{arctan}\left(\frac{x}{y}\right), & y < 0; \\ 0, x > 0, y = 0; \\ \pi, x < 0, y = 0; \\ \operatorname{undefined}, x = 0, y = 0. \end{cases}$$

# Algebraic form of complex number

$$(x + jy) + (a + jb) = (x + a) + j(y + b),$$
  

$$(x + jy)(a + jb) = (xa - yb) + j(xb + ya);$$
  

$$\frac{x + jy}{a + jb} = \frac{(x + jy)(a - jb)}{(a + jb)(a - jb)} = \frac{(xa + yb) + j(ay - xb)}{a^2 + b^2}.$$

Trigonometric form of the complex number



▲□▶ ▲圖▶ ▲≣▶ ▲≣▶ = 差 = のへで

### Impedance

Let us fix the law for the voltage:  $V = V_0 \cos(\omega t)$ . It is convenient to consider complex value

$$v(t) = V_0 e^{j\omega t}, \quad j^2 = -1.$$

In this case the Ohm law considered as follows

$$ir = v, \quad i = I_0 e^{j(\omega t - \phi)}.$$

Following parameter is called *impedance* :

$$r = rac{v}{i} = R_0 e^{j\phi}, \quad R_0 = \sqrt{R^2 + (\omega L - rac{1}{\omega C})^2}$$

The formula

$$v = ir, \quad r \in \mathbb{C}$$

can be considered as the Ohm law in a complex form.

### Impedance

The formula for the impedance in the algebraic form:

$$r = R + jZ, \quad Z = \omega L - \frac{1}{\omega C}.$$

The phase  $\phi$  can be obtained using a triangle where

$$\tan(\phi) = \frac{Z}{R}$$

The amplitude of the impedance is given by formula:

$$R_0 = \sqrt{R^2 + \left(\omega L - \frac{1}{C\omega}\right)^2}.$$

### Phasors

In the complex form for both the voltage and the current one can see the multiplier  $e^{i\omega t}$ :

$$v = V_0 e^{i\omega t}, \quad i = I_0 e^{j\phi} e^{i\omega t}.$$

・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・
 ・

This multiplier often neglected from the formulas for the current and voltage.

The multiplier  $e^{i\omega t}$  is called *phasor*.

Another phasor is the multiplier  $e^{j\phi}$ .

### Impedance for serial connection



For serial connected elements of AC circuit the capacity of the circuit:

$$\frac{1}{C\omega} = \sum_{I} \frac{1}{C_{I}\omega},$$

the inductivity of the circuit:

$$L=\sum_m L_m\omega,$$

and the resistance:

$$R=\sum_n R_n.$$

▲ロ ▶ ▲周 ▶ ▲ 国 ▶ ▲ 国 ▶ ● ○ ○ ○

### Impedance for serial connection

So the impedance is equal

$$r=R+j\left(L\omega-\frac{1}{C\omega}\right).$$

In general case  $r_k$  is the impedance of k-th element in the serial connected circuit:

$$r=\sum_{k}r_{k}.$$



#### Resistance:

$$R=R_1+R_2,$$

reactance is a difference of inductance and capacitance.

▲□▶ ▲□▶ ▲□▶ ▲□▶ ▲□ ● ● ●

Capacitance:

$$\frac{1}{\omega C} = \frac{1}{\omega C_2} + \frac{1}{\omega C_2} = \frac{C_1 C_2}{\omega (C_1 + C_2)},$$

Inductance:

 $L = L_1$ .

Impedance:

$$r = (R_1 + R_2) + j \left( L_1 \omega - \frac{(C_1 + C_2)}{\omega C_1 C_2} \right).$$

### Impedance for parallel connection

For parallel connection the same voltage for every line of connection. Every *k*-th line the complex form of the resistance is defined by

$$r_k = R_k + Z_k,$$

Therefore the Ohm law for every thread:

$$I_k r_k = V, \quad I_k = \frac{V}{r_k}.$$

 $Z_{k} = j\left(L_{k}\omega - \frac{1}{C_{k}\omega}\right).$ 

So for the circuit:

$$I = \sum I_k = \sum \frac{V}{r_k} = V \sum \frac{1}{r_k}.$$



Impedance of first thread:  $r_1 = R_1 + j\omega L_1$ . Impedance of second thread:  $r_2 = -\frac{j}{\omega C_2}$ . Impedance of third thread:  $r_3 = j\left(L_3 - \frac{1}{\omega C_3}\right)$ . Equivalent impedance:

$$\frac{1}{r} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} = \frac{r_1 r_2 + r_2 r_3 + r_3 r_1}{r_1 r_2 r_3}.$$

$$r = \frac{(R_1 + j\omega L_1)\frac{j}{\omega C_2} j\left(L_3 - \frac{1}{\omega C_3}\right)}{(R_1 + j\omega L_1)\frac{j}{\omega C_2} + \frac{j}{\omega C_2} j\left(L_3 - \frac{1}{\omega C_3}\right) + (R_1 + j\omega L_1)}.$$

$$r = -\frac{(R_1 + j\omega L_1)(L_1 - \frac{1}{\omega C_3})}{jR_1 - \omega L_1 - L_3 - \frac{1}{\omega C_3} + C_2\omega(R_1 + j\omega L_1)}.$$

・ロト・西・・日・・日・・日・ 今々ぐ

# Kirchhoff's laws for AC current



For any node of the circuit

$$\sum_k i_k = 0,$$

where  $i_k$  is the complex valued AC current on *k*-th wire. Every current can be written in the form:

$$i_k = I_k e^{j\phi_k} e^{j\omega t}$$

For sinusoidal current this yields:

$$\sum_{k} I_k e^{j\phi_k} e^{j\omega t} = 0, \quad e^{j\omega t} \sum_{k} I_k e^{j\phi_k} = 0.$$

In this case one get the sum of the currents for given node as a polygon.

$$\sum_{k} I_k e^{j\phi_k} = 0$$

# Kirchhoff's laws for AC current



For every mesh one get:

$$\sum_{k} \left( i_k R_k + L_k \frac{di_k}{dt} + \frac{1}{C_k} \int i_k dt \right) = \sum_{k} \mathcal{E}_k,$$

where  $R_k$  is resistance,  $L_k$  is a unductance,  $C_k$  is a capacitance and  $i_k$  is a current through given k-th thread and  $e_k$  is a source of voltage. For the sinusoidal current one get:

$$\sum_{k} I_{k} \left( R_{k} + L_{k} \omega e^{j\pi/2} - \frac{1}{\omega C_{k}} e^{-j\pi/2} \right) e^{j\omega t} = \sum_{k} e_{k} e^{j\omega t}.$$

$$\sum_{k} I_{k} \left( R_{k} + j \left( L_{k} \omega - \frac{1}{\omega C_{k}} \right) \right) = \sum_{k} e_{k}.$$

$$\sum_{k} I_{k} r_{k} = \sum_{k} e_{k}.$$



Let us consider the circuit.

Define the positive direction of the current  $I_1$ .

The voltage between pins *ab* and *ac* are defined as follows:

$$V_{ab} = I_1 R_1$$

and

$$V_{ac} = l_1 r_1 = l_1 (R_1 - j \frac{1}{\omega C_1}).$$

▲□▶ ▲□▶ ▲三▶ ▲三▶ 三三 のへで



The current  $I_2$  is orthogonal to ac and

$$I_2 = rac{V_{ac}}{r_{ac}}, \quad r_{ac} = j\omega L_2.$$



$$I_3 = I_1 + I_2$$
,  $V_{ad} = I_3 R_3$ ,  $V_{de} = -I_3 \frac{j}{\omega C_3}$ ,  $V_{ae} = I_3 (R_3 - \frac{j}{\omega C_3})$ .

◆□ ▶ ◆昼 ▶ ◆ 臣 ▶ ◆ 臣 ● の Q @



$$E_3 = V_{ac} - V_{ae}.$$

ヘロン ヘロン ヘヨン ヘヨン

æ



▲□▶ ▲□▶ ▲□▶ ▲□▶ ▲□ ● のへで

Final graph for the circuit.



▲□▶ ▲□▶ ▲□▶ ▲□▶ ▲□ ● のへで

Two diagrams are united each other.

# Summary

Impedance.

Kirchhoff laws and diagrams for currents and voltages.

(ロ)、(型)、(E)、(E)、 E) のQ(()